

Computer Architecture

ICT 1019Y Week 04 Lecture

Digital Logic

Combinational Circuits

Implementing Boolean Functions


- How do we **physically implement** Boolean functions?

$$F(X, Y, Z) = (X+Y) (X+\overline{Y}) (\overline{X}\overline{Z})$$

- Using digital computer circuits called **gates**
- What is a gate?
 - Electronic device that produces a result based on two or more input values
 - Built out of 1-6 transistors (but we'll treat a gate as a single fundamental unit in this class)
- Integrated circuits contain gates organized to accomplish a specific task

Gates: AND, OR, NOT


AND Gate

 

X AND Y

X	Y	XY
0	0	0
0	1	0
1	0	0
1	1	1


OR Gate

 

X OR Y

X	Y	X+Y
0	0	0
0	1	1
1	0	1
1	1	1

NOT Gate

 

NOT X


X	\bar{X}
0	1
1	0

Look at the NOT gate: The **○** symbol represents “NOT”. You’ll see it on other gates

Gates: XOR

Exclusive OR (XOR)

X XOR Y		
X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

 

- The output of the XOR operation is **true** only when the values of the **inputs are different**
- Note the special symbol \oplus for the XOR operation.


Gates: NAND, NOR

NAND (AND w/NOT)

➤ AND with NOT afterwards

$X \text{ NAND } Y$


X	Y	$X \text{ NAND } Y$
0	0	1
0	1	1
1	0	1
1	1	0

 

<

· *Normal form* ·

>

 

<

· *DeMorgan's Law
enables these
alternate forms* ·


>

NOR (OR w/NOT)

➤ OR with NOT afterwards

$X \text{ NOR } Y$

X	Y	$X \text{ NOR } Y$
0	0	1
0	1	0
1	0	0
1	1	0

 

Universal Gates

➤ Why bother with NAND and NOR?




➤ Don't they make our life more difficult compared to the obvious AND, OR, NOT?

➤ NAND and NOR are **universal gates**

➤ Easy to manufacture



➤ Any Boolean function can be constructed out of only NAND or only NOR gates

Example using only NAND gates:

   

Multiple Input / Multiple Output

  
- We can physically build many variations of these basic gates
 - Gates with many inputs? Yes!
 - Gates with many outputs? Yes!
 - Second output might be for the complement of the operation



Combining Gates

- Boolean functions can be implemented by combining many gates together

$$F(X, Y, Z) = X + \bar{Y}Z$$

 

- **Why did we simplify our Boolean expressions previously?**
 - So we can build simpler circuits with fewer gates!


Combinational Circuits



Combinational Circuits


- Two general classifications of circuits
 - **Combinational** logic circuits
 - **Sequential** logic circuits
- Combinational logic circuits
 - Produce a specified output (almost) at the instant when input values are applied
 - Also known as: “Combinatorial circuits”
- Sequential logic circuits
 - Incorporate delay/“memory” elements
 - Will discuss later

Combinational Circuit

 

➔ In teams of 2, write the truth table for this circuit

Combinational Circuit

 

x	y	z	A	B	C	D	F(x,y,z)
0	0	0	1	0	0	0	0
0	0	1	1	0	1	0	1
0	1	0	1	1	0	1	1
0	1	1	1	1	1	1	0
1	0	0	0	0	0	1	1
1	0	1	0	0	0	1	1
1	1	0	0	0	0	1	1
1	1	1	0	0	0	1	1

Combinational Circuit – Half Adder

➤ Half Adder


➤ Finds the sum of two bits

➤ How can I implement the truth table?

➤ $\text{Sum} = x \oplus y$ (XOR)

➤ $\text{Carry} = x \text{ AND } y$

Inputs		Outputs	
X	Y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

Combinational Circuit – Full Adder


- A **full adder** is a half adder plus the ability to process a **carry-input** bit

Inputs			Outputs	
X	Y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

New input: ▀

Combinational Circuit – Full Adder

 
➤ What do we need to add to the half adder (shown below) to make it a full adder?



Inputs			Outputs	
X	Y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Combinational Circuit – Full Adder

 
A Full Adder is really just two Half Adders in **series**



Inputs			Outputs	
X	Y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Ripple Carry Adder

 
- Full adders can be connected in series to form a ripple carry adder
 - The carry bit “ripples” from one adder to the next



- **Why is the performance of this approach slow?**
 - Slow due to long propagation paths
 - Modern systems use more efficient adders

Combinational Circuit – Decoder

 
➤ Selects one (of many) outputs from a single input



Combinational Circuit – Decoder

➤ Implementation of a 2 input to 4 output decoder

 **If $x = 0$ and $y = 1$,
which output line
is enabled?**



Memory

- Common **decoder** application: **Memory** address decoders
 - n inputs can select any of 2^n locations.
- Example: Suppose we build a memory that stores 2048 bytes using several 64x4 RAM chips
 - How do we determine **which RAM chip to use** when reading/writing a particular address?

Memory

Build this:

▪

Full Memory
2048 total bytes
*(or $2048 = 2^{11}$ addresses,
1 byte per address)*

^^^ ^^

vvv vvv

Data wires
(8)

^ ^^^ ^^^ ^

v vvvvv vvvvv

Address wires
(11)

With many of these:

▪

64x4 RAM Chip
64 (or 2^6) locations
4 bits per location

^^^^

vvvv

Data wires
(4)

^^^^ ^

vvvvv


Address wires
(6)

Memory

- To get 2048 total addresses, we need $2048/64 = \mathbf{32 \text{ banks}}$ of RAM chips
- To make each address contains one byte (8 bits) we must access $8/4 = 2$ chips in parallel
 - Therefore, a total of $32*2 = \mathbf{64 \text{ RAM chips}}$
 - Picture an array of RAM chips
 - 32 rows
 - 2 columns
- To determine which of 32 possible banks to read data from, a 5-to-32 decoder is needed ($2^5 = 32$)


Combinational Circuit – Multiplexer

 - A **multiplexer** selects a single output from several inputs
- Which input is chosen?
 - Selected by the value on the multiplexer's control lines
- To select from n inputs, $\log_2 n$ control lines are needed.



Combinational Circuit – Multiplexer

➤ Implementation of a 4-to-1 multiplexer

 


If $S_0 = 1$ and $S_1 = 0$,
which input is
transferred to the
output?

Combinational Circuit – Shifter

➤ This **shifter** moves the bits of a 4-bit input one position to the left or right

➤ If $S = 0$, in which direction do the input bits shift?

➤ Left!

 

Combinational Circuits

- **Does the output of a combinational circuit change instantly when the input changes?**
 - No – takes a tiny (but measurable) length of time
 - Electrical signals in a wire have a finite speed
 - A transistor takes a finite time to change state

Recap

➤ What is the difference between a decoder and a multiplexer?

